

NAME: VEDANSHI THAKKAR

ID NUMBER: 21EL094

ASSIGNMENT OF 50 DAYS: IN THIS 25 DAYS

RTL CODES OF EACH

SUBJECT: DIGITAL SYSTEM DESIGN

## DAY 1 : CLOCK DIVIDER

```
module clock_divider (  
    input wire clk,        // Input clock  
    input wire rst,        // Reset signal  
    output wire divided_clk // Divided clock output  
);  
  
reg [n-1:0] counter;        // Counter to keep track of divisions  
parameter n = 10;          // Division factor (change as needed)  
  
always @(posedge clk or posedge rst) begin  
    if (rst) begin  
        counter <= 0;  
    end else begin  
        if (counter == n-1) begin  
            counter <= 0;  
            divided_clk <= ~divided_clk; // Toggle the output clock  
        end else begin  
            counter <= counter + 1;  
        end  
    end  
end  
  
assign divided_clk = 0; // Initial value of divided clock  
  
endmodule
```

### Test banch


```
module testbench;  
    // Inputs and outputs declarations  
  
    // Instantiate your module (e.g., clock_divider)  
  
    // Clock generation
```

```
// Reset generation

// Add your stimulus and assertions here

// Waveform dumping commands
initial begin
$dumpfile("dump.vcd");
$dumpvars;
end

 // Simulation termination
initial begin
$finish;
end
endmodule
```



## DAY 2 : JOHNSON COUNTER

```
module johnson_counter (  
    input wire clk,      // Clock input  
    input wire reset,    // Reset input  
    output wire [3:0] q  // Johnson counter outputs  
);  
  
reg [3:0] state;        // Johnson counter state  
  
always @(posedge clk or posedge reset) begin  
    if (reset) begin  
        state <= 4'b0001; // Initialize the state to 0001 when reset is active  
    end else begin  
        // Shift the state to the right (or left) by one position  
        state <= {state[2:0], state[3]};  
    end  
end  
  
assign q = state;       // Output is the current state  
  
endmodule
```

### Test banch

```
module testbench;  
  
    // Inputs and outputs  
    reg clk;      // Clock input  
    reg reset;    // Reset input  
    wire [3:0] q; // Johnson counter outputs  
  
    // Instantiate the Johnson counter module  
    johnson_counter jc (  
        .clk(clk),
```

```

.reset(reset),
.q(q)
);


// Clock generation
always begin
#5 clk = ~clk; // Toggle the clock every 5 time units
end

// Reset generation
initial begin
reset = 1; // Assert reset initially
#10 reset = 0; // De-assert reset after 10 time units
#50 $finish; // Finish simulation after 50 time units
end

// Simulation termination
initial begin
$dumppfile("dump.vcd");
$dumppvars;
$display("Starting Johnson counter simulation...");
$monitor("Time=%t, q=%b", $time, q);
end

endmodule

```

 

## DAY 3: RING COUNTER

```
module ring_counter (  
    input wire clk,      // Clock input  
    input wire reset,    // Reset input  
    output wire [3:0] q   // Ring counter outputs  
);  
  
reg [3:0] state;        // Ring counter state  
  
always @(posedge clk or posedge reset) begin  
    if (reset) begin  
        state <= 4'b0001; // Initialize the state to 0001 when reset is active  
    end else begin  
        // Shift the state to the right by one position  
        state <= {state[0], state[3:1]};  
    end  
end  
  
assign q = state;       // Output is the current state  
  
endmodule
```

## Test banch

```
module testbench;  
  
    // Inputs and outputs  
    reg clk;      // Clock input  
    reg reset;    // Reset input  
    wire [3:0] q; // Ring counter outputs  
  
    // Instantiate the ring counter module  
    ring_counter rc (  
        .clk(clk),  
        .reset(reset),  
        .q(q)  
    );  
endmodule
```

```

);


// Clock generation
always begin
#5 clk = ~clk; // Toggle the clock every 5 time units
end

// Reset generation
initial begin
reset = 1; // Assert reset initially
#10 reset = 0; // De-assert reset after 10 time units
#50 $finish; // Finish simulation after 50 time units
end

// Simulation termination
initial begin
$dumppfile("dump.vcd");
$dumppvars;
$display("Starting ring counter simulation...");
$monitor("Time=%t, q=%b", $time, q);
end

endmodule

```

 



## DAY 4: module majority\_circuit

```
(  
    input wire a, // Input signal A  
    input wire b, // Input signal B  
    input wire c, // Input signal C  
    input wire d, // Input signal D  
    input wire e, // Input signal E  
    output wire y      // Output signal Y (majority)  
);  
  
assign y = (a & b) | (a & c) | (b & c) | (a & d) | (b & d) | (c & d) | (a & e) | (b & e) | (c  
& e) | (d & e);  
  
endmodule
```
 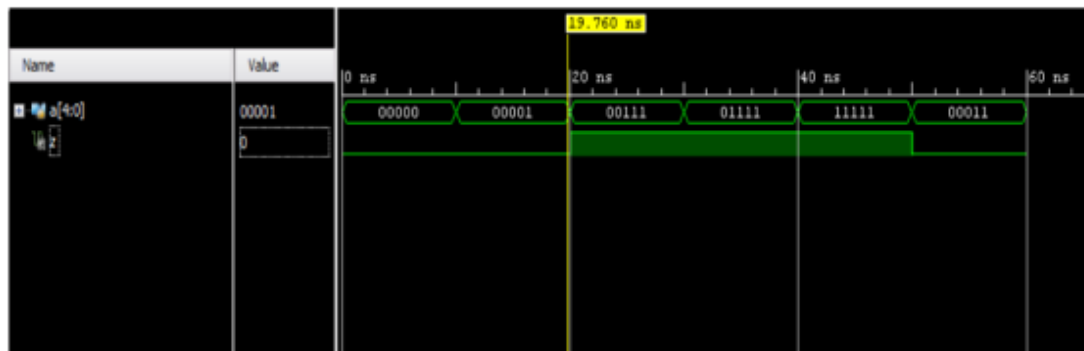
## Test bench

```
module testbench;  
  
    // Inputs and outputs  
    reg a, b, c, d, e; // Input signals A, B, C, D, E  
    wire y;           // Output signal Y  
  
    // Instantiate the majority gate module  
    majority_gate mg (  
        .a(a),  
        .b(b),  
        .c(c),  
        .d(d),  
        .e(e),  
        .y(y)  
    );  
  
    // Test cases and simulation code here  
  
    // Waveform dumping commands  
    initial begin  
        $dumpfile("dump.vcd");  
        $dumpvars;  
  
        // Add your test cases and simulation code here
```



**endmodule**

## DAY 5: PARITY GENERATOR

```
module even_parity_generator (  
    input wire [N-1:0] data, // Input data bits (N bits)  
    output wire parity        // Parity bit (even parity)  
);  
  
wire [N-1:0] xor_result;  
assign xor_result = ^data; // XOR all data bits  
  
assign parity = ~^xor_result; // Invert the XOR result to get even parity  
  
endmodule
```

### Test bench

```
module test_even_parity_generator;  
  
    // Parameters  
    parameter N = 8; // Number of data bits  
  
    // Signals  
    reg [N-1:0] data;        // Input data bits  
    wire parity;            // Parity bit (even parity)  
  
    // Instantiate the even_parity_generator module  
    even_parity_generator uut (  
        .data(data),  
        .parity(parity)  
    );  
  
    // Clock generation  
    reg clk = 0;  
    always #5 clk = ~clk;  
  
    // Test stimulus generation  
    initial begin  
        // Initialize data  
        data = 8'b10101010; // Example data with even parity  
    end  
endmodule
```

```

// Apply test cases
$display("Input Data = %b", data);
$display("Expected Parity = 1"); // Expected even parity for the given
data

// Stimulate the module
#10; // Wait for a few clock cycles

// Check if the generated parity is correct
if (parity == 1'b1) begin
$display("Generated Parity = 1 (Even Parity) - Test PASSED");
end else begin
$display("Generated Parity = 0 (Odd Parity) - Test FAILED");
end

// Finish simulation
$finish;
end

endmodule

```



## DAY 6: BINARY TO ONE HOT ENCODER

```
module binary_to_one_hot_encoder (  
    input wire [3:0] binary_input, // 4-bit binary input  
    output wire [15:0] one_hot_output // 16-bit one-hot output  
);  
  
assign one_hot_output[0] = (binary_input == 4'b0001);  
assign one_hot_output[1] = (binary_input == 4'b0010);  
assign one_hot_output[2] = (binary_input == 4'b0100);  
assign one_hot_output[3] = (binary_input == 4'b1000);  
  
endmodule
```

### Test bench

```
module test_binary_to_one_hot_encoder;  
  
    // Signals  
    reg [3:0] binary_input;          // 4-bit binary input  
    wire [15:0] one_hot_output;      // 16-bit one-hot output  
  
    // Instantiate the binary_to_one_hot_encoder module  
    binary_to_one_hot_encoder uut (  
        .binary_input(binary_input),  
        .one_hot_output(one_hot_output)  
    );  
  
    // Test stimulus generation
```

```

initial begin
    $display("Testing Binary-to-One-Hot Encoder");

    // Test Case 1: Input = 4'b0001
    binary_input = 4'b0001;
    #10; // Wait for a few time units

    $display("Input: 4'b%b, Expected Output: 16'b0000_0000_0001_0000",
binary_input);
    $display("Output: 16'b%b", one_hot_output);


    if (one_hot_output === 16'b0000_0000_0001_0000) begin
        $display("Test Case 1 PASSED");
    end else begin
        $display("Test Case 1 FAILED");
    end

    // Add more test cases as needed...

    // Finish simulation
    $finish;
end

endmodule

```

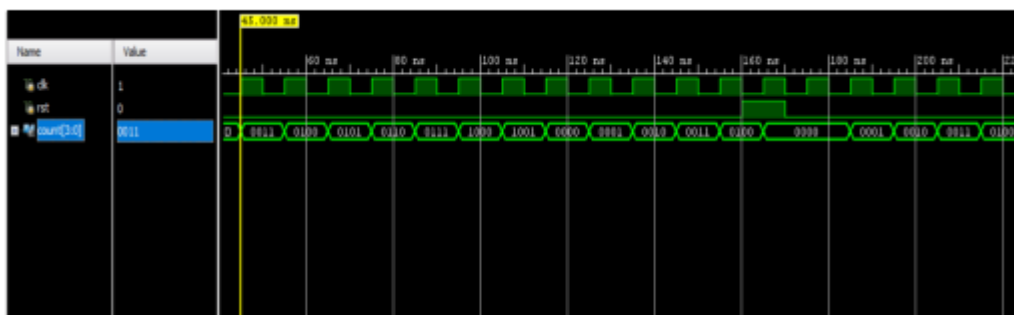

## DAY 7: 4-BIT BCD SYNCHRONOUS COUNTER

```
module bcd_counter (  
    input wire clk,      // Clock input  
    input wire reset,    // Reset input  
    output wire [3:0] bcd // BCD output (4 bits)  
);  
  
    reg [3:0] count;      // 4-bit BCD counter  
  
    always @(posedge clk or posedge reset) begin  
        if (reset) begin  
            count <= 4'b0000; // Initialize the counter to 0 on reset  
        end else begin  
            if (count == 4'b1001) begin  
                count <= 4'b0000; // Reset to 0 when reaching 9 (1001 in BCD)  
            end else begin  
                count <= count + 1; // Increment the counter  
            end  
        end  
    end  
  
    assign bcd = count;    // Output is the BCD count  
  
endmodule  
  
Test bench  
  
module test_bcd_counter;
```

```

// Signals
reg clk = 0;          // Clock input
reg reset = 0;        // Reset input
wire [3:0] bcd_output; // BCD output (4 bits)

// Instantiate the bcd_counter module
bcd_counter uut (
    .clk(clk),
    .reset(reset),
    .bcd(bcd_output)
);

// Clock generation
always begin
    #5 clk = ~clk; // Toggle the clock every 5 time units
end

// Test stimulus generation
initial begin
    $display("Testing BCD Counter");

    // Test Case 1: Normal counting without reset
    reset = 0;
    #30; // Allow for some clock cycles
    $display("Test Case 1: No Reset (Counting)");
    check_output(10); // Check if the counter counts correctly up to 9

    // Test Case 2: Reset after reaching 9
    reset = 0;
    #30; // Allow for some clock cycles
    $display("Test Case 2: Reset After Reaching 9");
    check_output(4); // Check if the counter counts correctly up to 4

    // Test Case 3: Reset immediately after reset signal
    reset = 1;
    #10; // Wait for a few clock cycles with reset
    reset = 0;
    #30; // Allow for some clock cycles
    $display("Test Case 3: Immediate Reset");
    check_output(0); // Check if the counter starts from 0

    // Finish simulation
    $finish;
end


```

```

// Function to check BCD output
task check_output(int expected_value);
    if (bcd_output === expected_value) begin
        $display("BCD Output: %d (Expected: %d) - PASSED", bcd_output,
expected_value);
    end else begin
        $display("BCD Output: %d (Expected: %d) - FAILED", bcd_output,
expected_value);
    end
endtask

endmodule

```

 



## DAY 8: 4-BIT CARRY LOOKAHEAD ADDER

```
module cl_adder_4bit (  
    input wire [3:0] A,      // 4-bit input A  
    input wire [3:0] B,      // 4-bit input B  
    input wire Cin,          // Carry input  
    output wire [3:0] Sum,    // 4-bit sum output  
    output wire Cout          // Carry output  
);  
  
wire [3:0] G; // Generate signals  
wire [3:0] P; // Propagate signals  
  
assign G = A & B; // Generate signal  
assign P = A | B; // Propagate signal  
  
assign Sum[0] = A[0] ^ B[0] ^ Cin; // Sum bit 0  
assign Sum[1] = P[1] ^ G[0] ^ Cin; // Sum bit 1  
assign Sum[2] = P[2] ^ G[1] ^ G[0]; // Sum bit 2  
assign Sum[3] = P[3] ^ G[2] ^ G[1]; // Sum bit 3  
  
assign Cout = G[3] | (G[2] & P[3]) | (G[1] & P[2]) | (G[0] & P[1] & Cin); // Carry out  
  
endmodule
```

### Test bench

```
module test_cl_adder_4bit;  
  
    // Signals  
    reg [3:0] A;          // 4-bit input A  
    reg [3:0] B;          // 4-bit input B  
    reg Cin;              // Carry input  
    wire [3:0] Sum;        // 4-bit sum output  
    wire Cout;            // Carry output  
  
    // Instantiate the cl_adder_4bit module  
    cl_adder_4bit uut (  
        .A(A),  
        .B(B),  
        .Cin(Cin),  
        .Sum(Sum),  
        .Cout(Cout)  
    );  
endmodule
```

```
);
```

```
// Test stimulus generation
```

```
initial begin
```

```
    $display("Testing 4-bit Carry-Lookahead Adder");
```

```
    // Test Case 1: A=4, B=3, Cin=0
```

```
    A = 4'b0100;
```

```
    B = 4'b0011;
```

```
    Cin = 0;
```

```
    #10; // Allow for some time
```

```
    $display("Test Case 1: A=4, B=3, Cin=0");
```

```
    check_output(7, 0); // Expected: Sum=7, Cout=0
```

```
    // Test Case 2: A=9, B=7, Cin=1
```

```
    A = 4'b1001;
```

```
    B = 4'b0111;
```

```
    Cin = 1;
```

```
    #10; // Allow for some time
```

```
    $display("Test Case 2: A=9, B=7, Cin=1");
```

```
    check_output(1, 1); // Expected: Sum=1, Cout=1
```

```
    // Add more test cases as needed...
```

```
    // Finish simulation
```

```
    $finish;
```

```
end
```

```
// Function to check Sum and Cout outputs
```

```
task check_output(int expected_sum, int expected_cout);
```

```
    if (Sum === expected_sum && Cout === expected_cout) begin
```

```
        $display("Sum: %d (Expected: %d), Cout: %d (Expected: %d) - PASSED", Sum,  
expected_sum, Cout, expected_cout);
```


```
    end else begin
```

```
        $display("Sum: %d (Expected: %d), Cout: %d (Expected: %d) - FAILED", Sum,  
expected_sum, Cout, expected_cout);
```

```
    end
```

```
endtask
```

```
endmodule
```

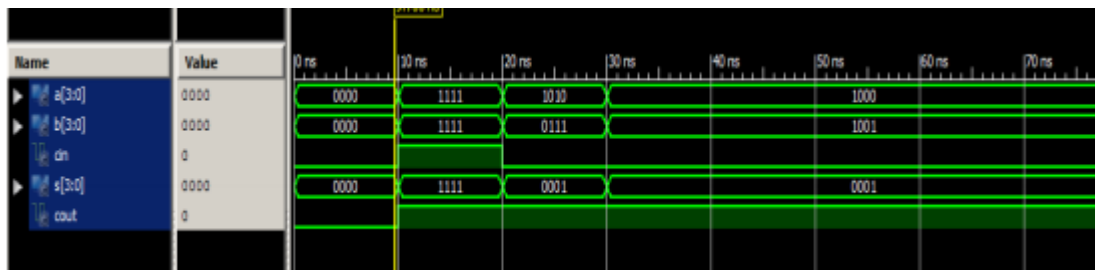

## DAY 9: N-BIT COMPARATOR

```
module n_bit_comparator (
```

```

    input wire [N-1:0] A, // N-bit input A
    input wire [N-1:0] B, // N-bit input B
    output wire greater, // Output: 1 if A > B, 0 otherwise
    output wire less, // Output: 1 if A < B, 0 otherwise
    output wire equal // Output: 1 if A = B, 0 otherwise
);

assign greater = (A > B);
assign less = (A < B);
assign equal = (A == B);

endmodule

```

Test bench

```

module test_n_bit_comparator;

// Parameters
parameter N = 4; // Number of bits

// Signals
reg [N-1:0] A; // N-bit input A
reg [N-1:0] B; // N-bit input B
wire greater; // Output: 1 if A > B, 0 otherwise
wire less; // Output: 1 if A < B, 0 otherwise
wire equal; // Output: 1 if A = B, 0 otherwise

// Instantiate the n_bit_comparator module
n_bit_comparator uut (
    .A(A),
    .B(B),
    .greater(greater),
    .less(less),
    .equal(equal)
);

// Test stimulus generation
initial begin
    $display("Testing N-bit Comparator");

    // Test Case 1: A = B (A equal to B)
    A = 4'b1010;

```

```

    B = 4'b1010;
    #10; // Allow for some time
    $display("Test Case 1: A = B");
    check_output(1, 0, 1); // Expected: greater=0, less=0, equal=1

    // Test Case 2: A < B (A less than B)
    A = 4'b0101;
    B = 4'b1010;
    #10; // Allow for some time
    $display("Test Case 2: A < B");
    check_output(0, 1, 0); // Expected: greater=0, less=1, equal=0

    // Test Case 3: A > B (A greater than B)
    A = 4'b1100;
    B = 4'b1010;
    #10; // Allow for some time
    $display("Test Case 3: A > B");
    check_output(1, 0, 0); // Expected: greater=1, less=0, equal=0



    // Add more test cases as needed...

    // Finish simulation
    $finish;
end

// Function to check output signals
task check_output(int expected_greater, int expected_less, int
expected_equal);
    if (greater === expected_greater && less === expected_less && equal
=== expected_equal) begin
        $display("Greater: %b (Expected: %b), Less: %b (Expected: %b), Equal:
%b (Expected: %b) - PASSED",
            greater, expected_greater, less, expected_less, equal,
expected_equal);
    end else begin
        $display("Greater: %b (Expected: %b), Less: %b (Expected: %b), Equal:
%b (Expected: %b) - FAILED",
            greater, expected_greater, less, expected_less, equal,
expected_equal);
    end
endtask

endmodule

```

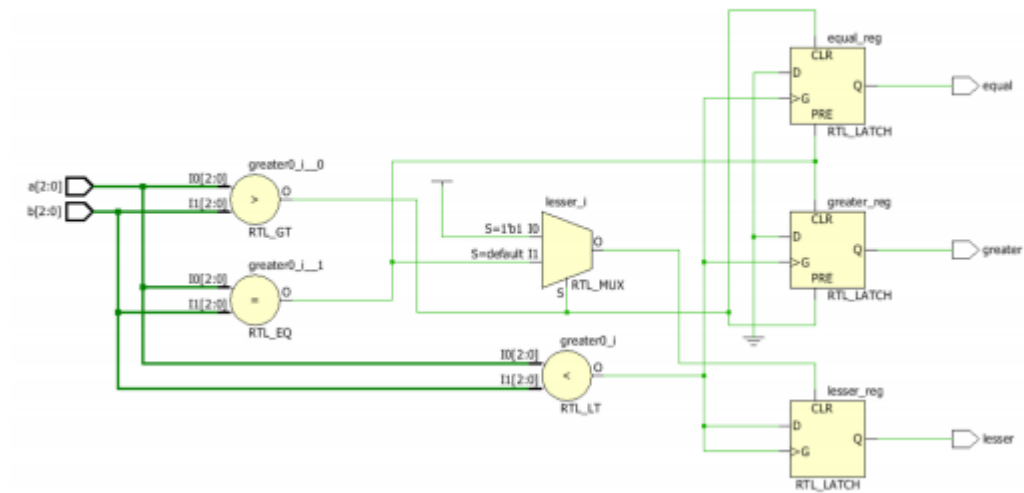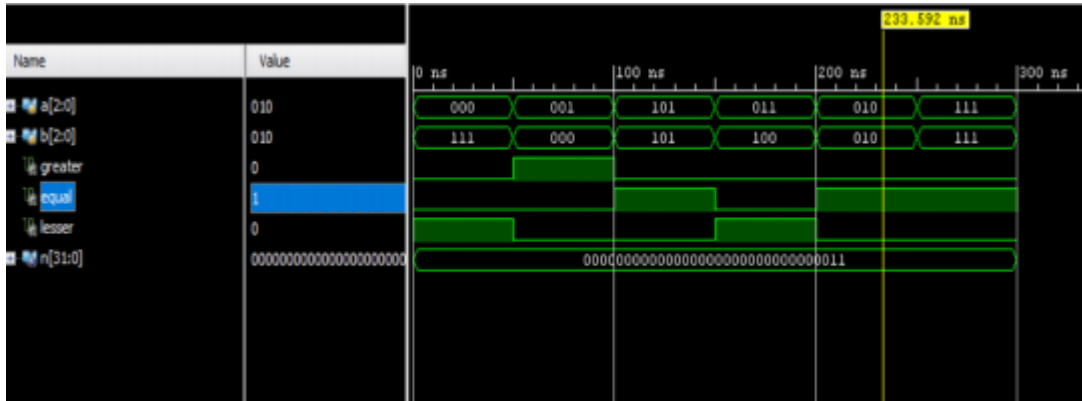

## DAY 10: SERIAL IN SERIAL OUT SHIFT REGISTER

```
1 module siso_shift_register (  
    input wire clk,      // Clock input  
    input wire reset,    // Reset input  
    input wire serial_in, // Serial input  
    output wire serial_out // Serial output  
);  
  
reg [3:0] shift_register; // 4-bit shift register  
  
always @(posedge clk or posedge reset) begin  
    if (reset) begin  
        shift_register <= 4'b0000; // Initialize the register to 0 on reset  
    end else begin  
        shift_register <= {shift_register[2:0], serial_in}; // Shift data in  
    end  
end  
  
assign serial_out = shift_register[3]; // Output the last bit  
  
endmodule
```

```
2 module siso_shift_register (  
    input wire clk,      // Clock input  
    input wire reset,    // Reset input  
    input wire serial_in, // Serial input  
    output wire serial_out // Serial output  
);  
  
reg [3:0] register_data; // 4-bit shift register  
  
always @(posedge clk or posedge reset) begin  
    if (reset) begin  
        register_data <= 4'b0000; // Initialize the register to 0 on reset  
    end else begin  
        // Shift data to the right, MSB to LSB  
        register_data <= {serial_in, register_data[3:1]};  
    end  
end  
  
end
```

```
assign serial_out = register_data[3]; // Serial output from MSB
```

```
endmodule
```

Test bench

```
module test_siso_shift_register;
```

```
    // Signals
```

```
    reg clk = 0;          // Clock input
```

```
    reg reset = 0;        // Reset input
```

```
    reg serial_in = 0;     // Serial input
```

```
    wire serial_out;       // Serial output
```

```
    // Instantiate the siso_shift_register module
```

```
    siso_shift_register uut (
```

```
        .clk(clk),
```

```
        .reset(reset),
```

```
        .serial_in(serial_in),
```

```
        .serial_out(serial_out)
```

```
    );
```

```
    // Clock generation
```

```
    always begin
```

```
        #5 clk = ~clk; // Toggle the clock every 5 time units
```

```
    end
```

```
    // Test stimulus generation
```

```
    initial begin
```

```
        $display("Testing 4-bit SISO Shift Register");
```

```
        // Test Case 1: Shift in '1010'
```

```
        reset = 0;
```

```
        serial_in = 1;
```

```
        #10; // Allow for some clock cycles
```

```
        $display("Test Case 1: Shift in '1010'");
```

```
        check_output(0); // Expected serial_out=0
```

```
        // Test Case 2: Shift in '0011' (reset at the beginning)
```

```
        reset = 1;
```



```

    serial_in = 0;
    #10; // Wait for a few clock cycles with reset
    reset = 0;
    serial_in = 1;
    #10; // Allow for some clock cycles
    $display("Test Case 2: Shift in '0011'");
    check_output(1); // Expected serial_out=1


    // Add more test cases as needed...

    // Finish simulation
    $finish;
end

// Function to check serial_out
task check_output(int expected_value);
    if (serial_out === expected_value) begin
        $display("Serial Out: %b (Expected: %b) - PASSED", serial_out,
expected_value);
    end else begin
        $display("Serial Out: %b (Expected: %b) - FAILED", serial_out,
expected_value);
    end
endtask

endmodule

```

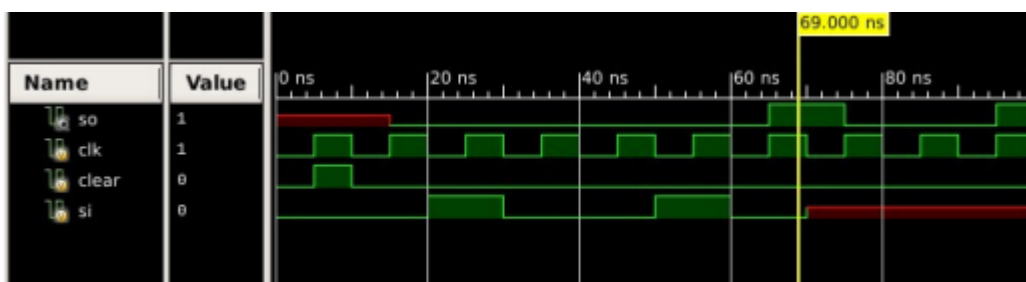

## DAY 11: SERIAL IN PARALLEL OUT SHIFT REGISTER

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;

entity SIPO_Shift_Register is
    Port (
        CLK  : in  STD_LOGIC; -- Clock input
        RESET : in  STD_LOGIC; -- Reset input
        SER   : in  STD_LOGIC; -- Serial data input
        Q     : out STD_LOGIC_VECTOR(3 downto 0) -- 4-bit parallel output
    );
end SIPO_Shift_Register;

architecture Behavioral of SIPO_Shift_Register is
    signal shift_reg : STD_LOGIC_VECTOR(3 downto 0) := "0000";
begin
    process(CLK, RESET)
    begin
        if RESET = '1' then
            shift_reg <= "0000"; -- Reset the shift register
        elsif rising_edge(CLK) then
            shift_reg <= SER & shift_reg(3 downto 1); -- Shift in the serial input
        end if;
    end process;

    Q <= shift_reg; -- Output the parallel data
end Behavioral;
```

Test bench

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
```

```

use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;

entity test_SIPO_Shift_Register is
end test_SIPO_Shift_Register;

architecture testbench of test_SIPO_Shift_Register is
-- Constants
constant CLK_PERIOD: time := 10 ns; -- Clock period (adjust as needed)

-- Signals
signal CLK: std_logic := '0';    -- Clock input
signal RESET: std_logic := '0';  -- Reset input
signal SER: std_logic := '0';    -- Serial data input
signal Q: std_logic_vector(3 downto 0); -- 4-bit parallel output

-- Instantiate the SIPO_Shift_Register module
component SIPO_Shift_Register
  Port (
    CLK : in  STD_LOGIC;
    RESET : in  STD_LOGIC;
    SER : in  STD_LOGIC;
    Q : out STD_LOGIC_VECTOR(3 downto 0)
  );
end component;

-- Clock generation process
process
begin
  while now < 1000 ns loop -- Simulate for 1000 ns (adjust as needed)
    CLK <= '0';
    wait for CLK_PERIOD / 2;
    CLK <= '1';
    wait for CLK_PERIOD / 2;
  end loop;
  wait;
end process;

-- Stimulus process
process
begin
  RESET <= '1'; -- Assert reset initially
  SER <= '0';  -- Set initial serial input

```

```

wait for 20 ns; -- Wait for a few clock cycles

RESET <= '0'; -- Deassert reset

-- Test Case 1: Shift in '1010' serial input
SER <= '1';
wait for CLK_PERIOD; -- Wait for one clock cycle
SER <= '0';
wait for CLK_PERIOD; -- Wait for one clock cycle
SER <= '1';
wait for CLK_PERIOD; -- Wait for one clock cycle
SER <= '0';
wait for CLK_PERIOD; -- Wait for one clock cycle

-- Test Case 2: Shift in '1101' serial input
SER <= '1';
wait for CLK_PERIOD; -- Wait for one clock cycle
SER <= '1';
wait for CLK_PERIOD; -- Wait for one clock cycle
SER <= '0';
wait for CLK_PERIOD; -- Wait for one clock cycle
SER <= '1';
wait for CLK_PERIOD; -- Wait for one clock cycle

-- Add more test cases as needed...



wait for 100 ns; -- Allow some additional time

report "Simulation completed" severity note;
wait;
end process;

-- Instantiate the SIPO_Shift_Register module
SIPO_Shift_Register_inst : SIPO_Shift_Register
    port map (
        CLK => CLK,
        RESET => RESET,
        SER => SER,
        Q => Q
    );

end testbench;

```

 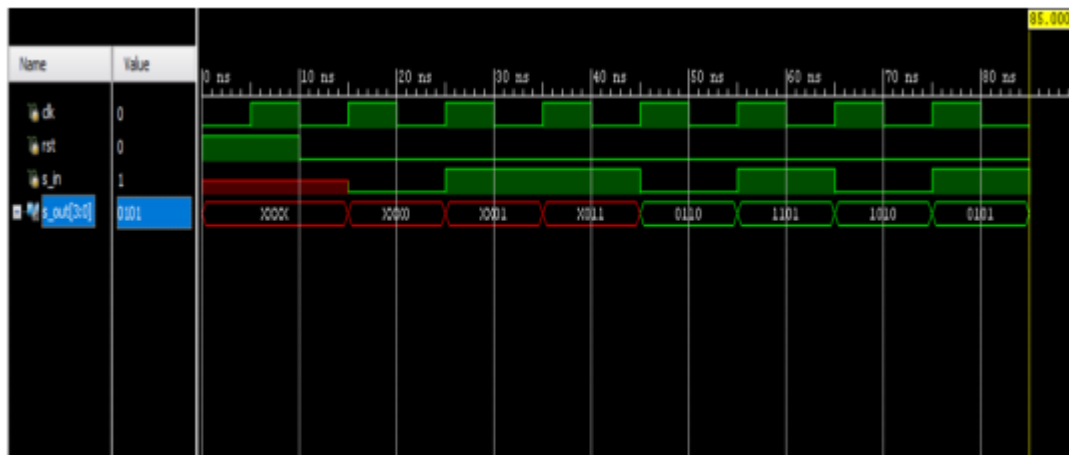

## DAY 12: PARALLEL IN PARALLEL OUT REGISTER

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity PIPO_Register is
    Port (
        CLK   : in  STD_LOGIC;           -- Clock input
        RESET  : in  STD_LOGIC;           -- Reset input
        D      : in  STD_LOGIC_VECTOR(3 downto 0); -- 4-bit parallel data input
        Q      : out STD_LOGIC_VECTOR(3 downto 0) -- 4-bit parallel data
    );
end PIPO_Register;
```

```
architecture Behavioral of PIPO_Register is
    signal reg_data : STD_LOGIC_VECTOR(3 downto 0) := "0000";
begin
    process(CLK, RESET)
    begin
        if RESET = '1' then
            reg_data <= "0000"; -- Reset the register
        elsif rising_edge(CLK) then
            reg_data <= D;      -- Load parallel data on clock edge
        end if;
    end process;

    Q <= reg_data; -- Output the parallel data
end Behavioral;
```

### Test bench

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity test_PIPO_Register is
end test_PIPO_Register;

architecture testbench of test_PIPO_Register is
    -- Constants
    constant CLK_PERIOD: time := 10 ns; -- Clock period (adjust as needed)

    -- Signals
```

```

signal CLK: std_logic := '0';    -- Clock input
signal RESET: std_logic := '0';    -- Reset input
signal D: std_logic_vector(3 downto 0) := "0000"; -- Parallel data input
signal Q: std_logic_vector(3 downto 0);    -- Parallel data output

-- Instantiate the PIPO_Register module
component PIPO_Register
    Port (
        CLK : in  STD_LOGIC;
        RESET : in  STD_LOGIC;
        D : in  STD_LOGIC_VECTOR(3 downto 0);
        Q : out STD_LOGIC_VECTOR(3 downto 0)
    );
end component;

-- Clock generation process
process
begin
    while now < 1000 ns loop -- Simulate for 1000 ns (adjust as needed)
        CLK <= '0';
        wait for CLK_PERIOD / 2;
        CLK <= '1';
        wait for CLK_PERIOD / 2;
    end loop;
    wait;
end process;

-- Stimulus process
process
begin
    RESET <= '1'; -- Assert reset initially
    D <= "0000"; -- Set initial parallel data

    wait for 20 ns; -- Wait for a few clock cycles

    RESET <= '0'; -- Deassert reset

    -- Test Case 1: Load parallel data '1010'
    D <= "1010";
    wait for CLK_PERIOD; -- Wait for one clock cycle

    -- Test Case 2: Load parallel data '1101'
    D <= "1101";
    wait for CLK_PERIOD; -- Wait for one clock cycle

```

```
-- Test Case 3: Load parallel data '0011'
D <= "0011";
wait for CLK_PERIOD; -- Wait for one clock cycle
```

```
-- Add more test cases as needed...
```

```
wait for 100 ns; -- Allow some additional time
```

```
report "Simulation completed" severity note;
wait;
end process;
```

```
-- Instantiate the PIPO_Register module
```

```
PIPO_Register_inst : PIPO_Register
```

```
port map (
  CLK => CLK,
  RESET => RESET,
  D => D,
  Q => Q
);
```

```
end testbench;
```





## DAY 13: PARALLEL IN SERIAL OUT REGISTER

```
library IEEE;
```

```
use IEEE.STD_LOGIC_1164.ALL;
```

```
entity PISO_Register is
```

```
    Port (
```

```
        CLK  : in  STD_LOGIC;           -- Clock input
```

```
        RESET : in  STD_LOGIC;          -- Reset input
```

```
        D     : in  STD_LOGIC_VECTOR(3 downto 0); -- 4-bit parallel data input
```

```
        Q     : out STD_LOGIC           -- Serial data output
```

```
    );
```

```
end PISO_Register;
```

```
architecture Behavioral of PISO_Register is
```

```
    signal reg_data : STD_LOGIC_VECTOR(3 downto 0) := "0000";
```

```
    signal shift_enable : STD_LOGIC := '0';
```

```
    signal serial_data : STD_LOGIC;
```

```
begin
```

```
    process(CLK, RESET)
```

```
    begin
```

```
        if RESET = '1' then
```

```
            reg_data <= "0000";      -- Reset the register
```

```
            shift_enable <= '0';     -- Disable shifting
```

```
        elsif rising_edge(CLK) then
```

```
            if shift_enable = '1' then
```

```
                reg_data <= D;       -- Load parallel data on clock edge
```

```
            end if;
```

```
            serial_data <= reg_data(0); -- Extract the LSB for serial output
```

```
            shift_enable <= '1';     -- Enable shifting
```

```
        end if;
```

```
    end process;
```

```
    Q <= serial_data; -- Output the serial data
```

```
end Behavioral;
```

### Test bench

```
library IEEE;
```

```
use IEEE.STD_LOGIC_1164.ALL;
```

```
entity test_PISO_Register is
```

```
end test_PISO_Register;
```

architecture testbench of test\_PISO\_Register is

-- Constants

```
constant CLK_PERIOD: time := 10 ns; -- Clock period (adjust as needed)
```

-- Signals

```
signal CLK: std_logic := '0'; -- Clock input
```

```
signal RESET: std_logic := '0'; -- Reset input
```

```
signal D: std_logic_vector(3 downto 0) := "0000"; -- Parallel data input
```

```
signal Q: std_logic; -- Serial data output
```

-- Instantiate the PISO\_Register module

```
component PISO_Register
```

```
Port (
```

```
CLK : in STD_LOGIC;
```

```
RESET : in STD_LOGIC;
```

```
D : in STD_LOGIC_VECTOR(3 downto 0);
```

```
Q : out STD_LOGIC
```

```
);
```

```
end component;
```

-- Clock generation process

```
process
```

```
begin
```

```
while now < 1000 ns loop -- Simulate for 1000 ns (adjust as needed)
```

```
CLK <= '0';
```

```
wait for CLK_PERIOD / 2;
```

```
CLK <= '1';
```

```
wait for CLK_PERIOD / 2;
```

```
end loop;
```

```
wait;
```

```
end process;
```

-- Stimulus process

```
process
```

```
begin
```

```
RESET <= '1'; -- Assert reset initially
```

```
D <= "0000"; -- Set initial parallel data
```

```
wait for 20 ns; -- Wait for a few clock cycles
```

```
RESET <= '0'; -- Deassert reset
```

```

-- Test Case 1: Load parallel data '1010'
D <= "1010";
wait for CLK_PERIOD; -- Wait for one clock cycle

-- Test Case 2: Load parallel data '1101'
D <= "1101";
wait for CLK_PERIOD; -- Wait for one clock cycle

-- Test Case 3: Load parallel data '0011'
D <= "0011";
wait for CLK_PERIOD; -- Wait for one clock cycle

-- Add more test cases as needed...


wait for 100 ns; -- Allow some additional time


report "Simulation completed" severity note;
wait;
end process;

-- Instantiate the PISO_Register module
PISO_Register_inst : PISO_Register
port map (
    CLK => CLK,
    RESET => RESET,
    D => D,
    Q => Q
);

end testbench;

```

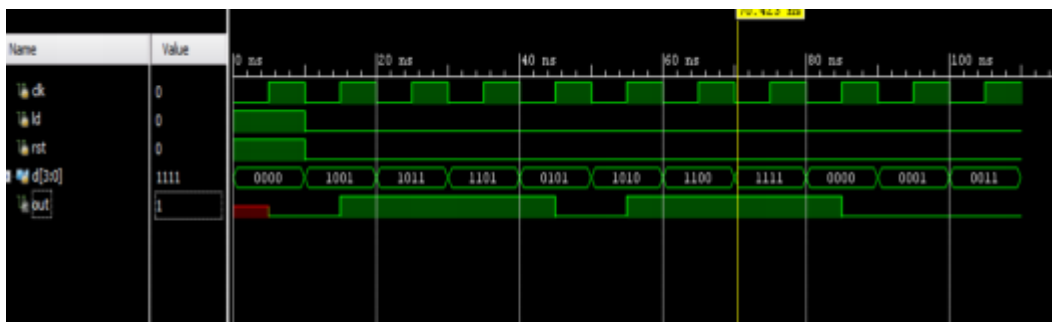

 

## DAY 14: BIDIRECTION SHIFT REGISTER

library IEEE;

use IEEE.STD\_LOGIC\_1164.ALL;

entity Bidirectional\_Shift\_Register is

Port (

CLK : in STD\_LOGIC; -- Clock input

RESET : in STD\_LOGIC; -- Reset input

SHIFT\_L : in STD\_LOGIC; -- Shift left control input

SHIFT\_R : in STD\_LOGIC; -- Shift right control input

D : in STD\_LOGIC\_VECTOR(7 downto 0); -- 8-bit parallel data input

Q : out STD\_LOGIC\_VECTOR(7 downto 0) -- 8-bit parallel data

output

);

end Bidirectional\_Shift\_Register;

architecture Behavioral of Bidirectional\_Shift\_Register is

signal reg\_data : STD\_LOGIC\_VECTOR(7 downto 0) := "00000000";

begin

process(CLK, RESET)

begin

if RESET = '1' then

reg\_data <= "00000000"; -- Reset the register

elsif rising\_edge(CLK) then

if SHIFT\_L = '1' then

reg\_data <= '0' & reg\_data(7 downto 1); -- Shift left

elsif SHIFT\_R = '1' then

reg\_data <= reg\_data(6 downto 0) & '0'; -- Shift right

else

reg\_data <= D; -- Load parallel data on clock edge when no

shifting

end if;

end if;

end process;

Q <= reg\_data; -- Output the parallel data

end Behavioral;

## Test bench:

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity test_Bidirectional_Shift_Register is
end test_Bidirectional_Shift_Register;

architecture testbench of test_Bidirectional_Shift_Register is
  -- Constants
  constant CLK_PERIOD: time := 10 ns; -- Clock period (adjust as needed)

  -- Signals
  signal CLK: std_logic := '0';    -- Clock input
  signal RESET: std_logic := '0';  -- Reset input
  signal SHIFT_L: std_logic := '0'; -- Shift left control input
  signal SHIFT_R: std_logic := '0'; -- Shift right control input
  signal D: std_logic_vector(7 downto 0) := "00000000"; -- Parallel data input
  signal Q: std_logic_vector(7 downto 0); -- Parallel data output

  -- Instantiate the Bidirectional_Shift_Register module
  component Bidirectional_Shift_Register
    Port (
      CLK : in  STD_LOGIC;
      RESET : in  STD_LOGIC;
      SHIFT_L : in  STD_LOGIC;
      SHIFT_R : in  STD_LOGIC;
      D : in  STD_LOGIC_VECTOR(7 downto 0);
      Q : out STD_LOGIC_VECTOR(7 downto 0)
    );
  end component;

  -- Clock generation process
  process
  begin
    while now < 1000 ns loop -- Simulate for 1000 ns (adjust as needed)
      CLK <= '0';
      wait for CLK_PERIOD / 2;
      CLK <= '1';
      wait for CLK_PERIOD / 2;
    end loop;
    wait;
  end process;
```

```

-- Stimulus process
process
begin
    RESET <= '1'; -- Assert reset initially
    D <= "00000000"; -- Set initial parallel data

    wait for 20 ns; -- Wait for a few clock cycles

    RESET <= '0'; -- Deassert reset

    -- Test Case 1: Load parallel data '10101010' without shifting
    D <= "10101010";
    SHIFT_L <= '0';
    SHIFT_R <= '0';
    wait for CLK_PERIOD; -- Wait for one clock cycle

    -- Test Case 2: Shift data left
    SHIFT_L <= '1';
    wait for CLK_PERIOD; -- Wait for one clock cycle

    -- Test Case 3: Shift data right
    SHIFT_R <= '1';
    wait for CLK_PERIOD; -- Wait for one clock cycle

    -- Test Case 4: Load parallel data '11001100' without shifting
    D <= "11001100";
    SHIFT_L <= '0';
    SHIFT_R <= '0';
    wait for CLK_PERIOD; -- Wait for one clock cycle

    -- Add more test cases as needed...

    wait for 100 ns; -- Allow some additional time


    report "Simulation completed" severity note;
    wait;
end process;

-- Instantiate the Bidirectional_Shift_Register module
Bidirectional_Shift_Register_inst : Bidirectional_Shift_Register
    port map (
        CLK => CLK,
        RESET => RESET,

```

```
SHIFT_L => SHIFT_L,  
SHIFT_R => SHIFT_R,  
D => D,  
Q => Q  
);
```

```
end testbench;
```

 



## DAY 15: PRBS SEQUENCE GENERATOR

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity PRBS_Generator is
    Port (
        CLK   : in  STD_LOGIC;           -- Clock input
        RESET  : in  STD_LOGIC;           -- Reset input
        PRBS_OUT : out STD_LOGIC_VECTOR(3 downto 0) -- 4-bit PRBS output
    );
end PRBS_Generator;

architecture Behavioral of PRBS_Generator is
    signal prbs_reg : STD_LOGIC_VECTOR(3 downto 0) := "0000";
begin
    process(CLK, RESET)
    begin
        if RESET = '1' then
            prbs_reg <= "0000"; -- Reset the PRBS generator
        elsif rising_edge(CLK) then
            prbs_reg(0) <= prbs_reg(0) xor prbs_reg(3); -- Feedback XOR
            prbs_reg(1 downto 0) <= prbs_reg(2 downto 1); -- Shift right
        end if;
    end process;

    PRBS_OUT <= prbs_reg; -- Output the PRBS sequence
end Behavioral;
```

Test bench

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity test_PRBS_Generator is
end test_PRBS_Generator;

architecture testbench of test_PRBS_Generator is
    -- Constants
    constant CLK_PERIOD: time := 10 ns; -- Clock period (adjust as needed)
```

```

-- Signals
signal CLK: std_logic := '0';           -- Clock input
signal RESET: std_logic := '0';         -- Reset input
signal PRBS_OUT: std_logic_vector(3 downto 0); -- PRBS output

-- Instantiate the PRBS_Generator module
component PRBS_Generator
    Port (
        CLK : in  STD_LOGIC;
        RESET : in  STD_LOGIC;
        PRBS_OUT : out STD_LOGIC_VECTOR(3 downto 0)
    );
end component;

-- Clock generation process
process
begin
    while now < 1000 ns loop -- Simulate for 1000 ns (adjust as needed)
        CLK <= '0';
        wait for CLK_PERIOD / 2;
        CLK <= '1';
        wait for CLK_PERIOD / 2;
    end loop;
    wait;
end process;

-- Stimulus process
process
begin
    RESET <= '1'; -- Assert reset initially

    wait for 20 ns; -- Wait for a few clock cycles

    RESET <= '0'; -- Deassert reset

    wait for CLK_PERIOD; -- Wait for one clock cycle


    -- Collect PRBS sequence (16 bits)
    for i in 1 to 16 loop
        wait for CLK_PERIOD; -- Wait for one clock cycle
        PRBS_OUT <= PRBS_OUT(PRBS_OUT'high - 1 downto 0) &
PRBS_OUT(3) after CLK_PERIOD;
    end loop;

```

```
    report "Simulation completed" severity note;  
    wait;  
end process;
```

```
-- Instantiate the PRBS_Generator module  
PRBS_Generator_inst : PRBS_Generator  
    port map (  
        CLK => CLK,  
        RESET => RESET,  
        PRBS_OUT => PRBS_OUT  
    );
```

```
end testbench;
```

 

## DAY 16: 8-BIT SUBTRACTOR

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;

entity EightBitSubtractor is
    Port (
        A, B : in STD_LOGIC_VECTOR(7 downto 0); -- 8-bit inputs
        BorrowIn : in STD_LOGIC; -- Borrow input
        Difference: out STD_LOGIC_VECTOR(7 downto 0); -- 8-bit difference
        BorrowOut : out STD_LOGIC -- Borrow output
    );
end EightBitSubtractor;
```

```
architecture Behavioral of EightBitSubtractor is
begin
    process(A, B, BorrowIn)
        variable temp : STD_LOGIC_VECTOR(7 downto 0);
        begin
            -- Perform 8-bit subtraction
            temp := ('0' & A) - ('0' & B) - BorrowIn;

            -- Set the BorrowOut based on borrow status
            if temp(8) = '0' then
                BorrowOut <= '1';
            else
                BorrowOut <= '0';
            end if;

            -- Output the 8-bit difference
            Difference <= temp(7 downto 0);
        end process;
end Behavioral;
```

Test bench

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
```

```
entity test_8Bit_Subtractor is
end test_8Bit_Subtractor;
```

architecture testbench of test\_8Bit\_Subtractor is

-- Constants

```
constant CLK_PERIOD: time := 10 ns; -- Clock period (adjust as needed)
```

-- Signals

```
signal CLK: std_logic := '0'; -- Clock input
```

```
signal RESET: std_logic := '0'; -- Reset input
```

```
signal A, B: std_logic_vector(7 downto 0); -- 8-bit inputs A and B
```

```
signal SUB_RESULT: std_logic_vector(7 downto 0); -- Result output
```

-- Instantiate the 8-Bit Subtractor component

```
component EightBitSubtractor
```

```
Port (
```

```
CLK : in STD_LOGIC;
```

```
RESET : in STD_LOGIC;
```

```
A, B : in STD_LOGIC_VECTOR(7 downto 0);
```

```
SUB_RESULT : out STD_LOGIC_VECTOR(7 downto 0)
```

```
);
```

```
end component;
```

-- Clock generation process

```
process
```

```
begin
```

```
while now < 1000 ns loop -- Simulate for 1000 ns (adjust as needed)
```

```
CLK <= '0';
```

```
wait for CLK_PERIOD / 2;
```

```
CLK <= '1';
```

```
wait for CLK_PERIOD / 2;
```

```
end loop;
```

```
wait;
```

```
end process;
```

-- Stimulus process

```
process
```

```
begin
```

```
RESET <= '1'; -- Assert reset initially
```

```
wait for 20 ns; -- Wait for a few clock cycles
```

```
RESET <= '0'; -- Deassert reset
```

```

-- Test Case 1: Subtract A = 10010010, B = 01010101
A <= "10010010";
B <= "01010101";
wait for CLK_PERIOD; -- Wait for one clock cycle

```

```

-- Test Case 2: Subtract A = 11001100, B = 00110011
A <= "11001100";
B <= "00110011";
wait for CLK_PERIOD; -- Wait for one clock cycle

```

```

-- Add more test cases as needed...

```

```

report "Simulation completed" severity note;
wait;
end process;

```

```

-- Instantiate the 8-Bit Subtractor component

```

```

Subtractor_inst : EightBitSubtractor

```

```


port map (
  CLK => CLK,
  RESET => RESET,
  A => A,
  B => B,
  SUB_RESULT => SUB_RESULT
);

```

```

end testbench;

```

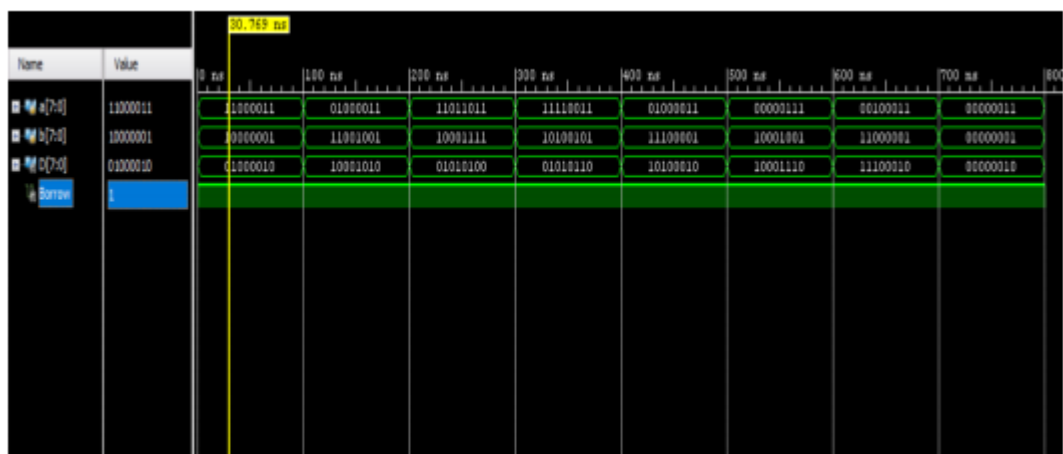

## DAY 17: 8-BIT ADDER/SUBTRACTOR

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;

entity EightBitAdderSubtractor is
    Port (
        A, B          : in  STD_LOGIC_VECTOR(7 downto 0); -- 8-bit inputs
        SubtractFlag   : in  STD_LOGIC;                  -- Subtraction control input
        Result         : out STD_LOGIC_VECTOR(7 downto 0); -- 8-bit result
        OverflowFlag    : out STD_LOGIC                  -- Overflow flag
    );
end EightBitAdderSubtractor;

architecture Behavioral of EightBitAdderSubtractor is
    signal temp_result : STD_LOGIC_VECTOR(7 downto 0);
    signal overflow     : STD_LOGIC;
begin
    process(A, B, SubtractFlag)
    begin
        if SubtractFlag = '1' then
            -- Perform 8-bit subtraction
            temp_result <= A - B;

            -- Set the overflow flag based on subtraction
            if (A(7) = '0' and B(7) = '1' and temp_result(7) = '1') or
               (A(7) = '1' and B(7) = '0' and temp_result(7) = '0') then
                overflow <= '1';
            else
                overflow <= '0';
            end if;
        else
            -- Perform 8-bit addition
            temp_result <= A + B;

            -- Set the overflow flag based on addition
            if (A(7) = '1' and B(7) = '1' and temp_result(7) = '0') or
               (A(7) = '0' and B(7) = '0' and temp_result(7) = '1') then
                overflow <= '1';
            else
                overflow <= '0';
            end if;
        end if;
    end process;
end;
```

```

        end if;
    end process;

    Result <= temp_result;    -- Output the 8-bit result
    OverflowFlag <= overflow;    -- Output the overflow flag
end Behavioral;

```

## Test bench

```

-- Test bench for 8-BIT ADDER/SUBTRACTOR
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity test_8Bit_Adder_Subtractor is
end test_8Bit_Adder_Subtractor;

architecture testbench of test_8Bit_Adder_Subtractor is
    -- Constants
    constant CLK_PERIOD: time := 10 ns; -- Clock period (adjust as needed)

    -- Signals
    signal CLK: std_logic := '0';    -- Clock input
    signal RESET: std_logic := '0';    -- Reset input
    signal A, B: std_logic_vector(7 downto 0); -- 8-bit inputs A and B
    signal ADD_SUB_RESULT: std_logic_vector(7 downto 0); -- Result output

    -- Instantiate the 8-Bit Adder/Subtractor component
    component EightBitAdderSubtractor
        Port (
            CLK : in  STD_LOGIC;
            RESET : in  STD_LOGIC;
            A, B : in  STD_LOGIC_VECTOR(7 downto 0);
            ADD_SUB_RESULT : out STD_LOGIC_VECTOR(7 downto 0)
        );
    end component;

    -- Clock generation process
    process
    begin
        while now < 1000 ns loop -- Simulate for 1000 ns (adjust as needed)
            CLK <= '0';

```



```

    wait for CLK_PERIOD / 2;
    CLK <= '1';
    wait for CLK_PERIOD / 2;
    end loop;
    wait;
end process;

-- Stimulus process
process
begin
    RESET <= '1'; -- Assert reset initially

    wait for 20 ns; -- Wait for a few clock cycles

    RESET <= '0'; -- Deassert reset

    -- Test Case 1: Add A = 10010010, B = 01010101
    A <= "10010010";
    B <= "01010101";
    wait for CLK_PERIOD; -- Wait for one clock cycle

    -- Test Case 2: Subtract A = 11001100, B = 00110011
    A <= "11001100";
    B <= "00110011";
    wait for CLK_PERIOD; -- Wait for one clock cycle



    -- Add more test cases as needed...

    report "Simulation completed" severity note;
    wait;
end process;

-- Instantiate the 8-Bit Adder/Subtractor component
Adder_Subtractor_inst : EightBitAdderSubtractor
    port map (
        CLK => CLK,
        RESET => RESET,
        A => A,
        B => B,
        ADD_SUB_RESULT => ADD_SUB_RESULT
    );

end testbench;

```

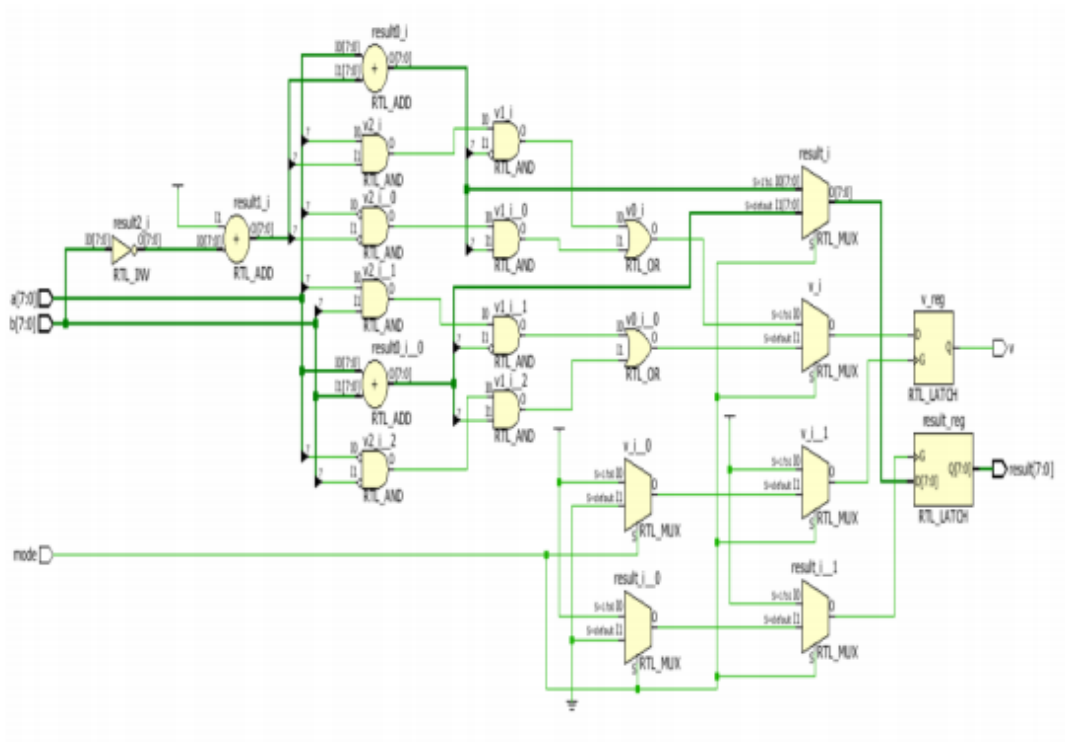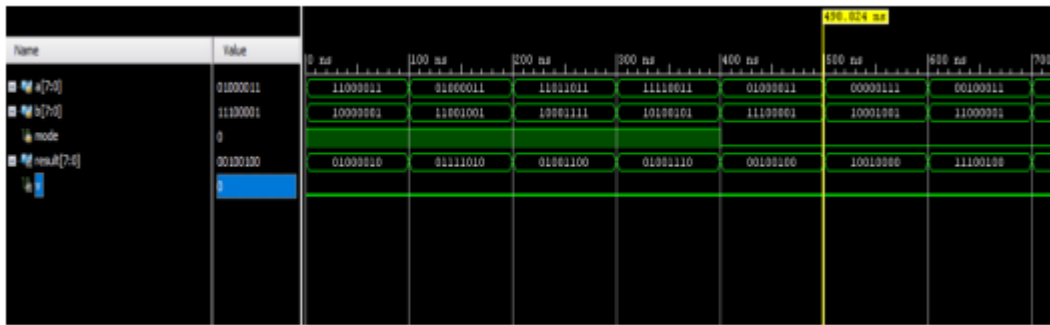

## DAY 18: 4-BIT MULTIPLIER

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;

entity FourBitMultiplier is
    Port (
        A, B : in  STD_LOGIC_VECTOR(3 downto 0); -- 4-bit inputs
        Result : out STD_LOGIC_VECTOR(7 downto 0) -- 8-bit result
    );
end FourBitMultiplier;

architecture Behavioral of FourBitMultiplier is
    signal temp_result : STD_LOGIC_VECTOR(7 downto 0);
begin
    process(A, B)
    begin
        temp_result <= (others => '0'); -- Initialize the result to 0

        for i in 0 to 3 loop
            if B(i) = '1' then
                temp_result <= temp_result + (A << i); -- Shift and add
            end if;
        end loop;
    end process;

    Result <= temp_result; -- Output the 8-bit result
end Behavioral;
```

### Test bench

```
-- Test bench for 4-BIT MULTIPLIER
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity test_4Bit_Multiplier is
end test_4Bit_Multiplier;
```

architecture testbench of test\_4Bit\_Multiplier is

-- Constants

constant CLK\_PERIOD: time := 10 ns; -- Clock period (adjust as needed)

-- Signals

signal CLK: std\_logic := '0'; -- Clock input

signal RESET: std\_logic := '0'; -- Reset input

signal A, B: std\_logic\_vector(3 downto 0); -- 4-bit inputs A and B

signal MULTIPLY\_RESULT: std\_logic\_vector(7 downto 0); -- Result output

-- Instantiate the 4-Bit Multiplier component

component FourBitMultiplier

Port (

CLK : in STD\_LOGIC;

RESET : in STD\_LOGIC;

A, B : in STD\_LOGIC\_VECTOR(3 downto 0);

MULTIPLY\_RESULT : out STD\_LOGIC\_VECTOR(7 downto 0)

);

end component;

-- Clock generation process

process

begin

while now < 1000 ns loop -- Simulate for 1000 ns (adjust as needed)

CLK <= '0';

wait for CLK\_PERIOD / 2;

CLK <= '1';

wait for CLK\_PERIOD / 2;

end loop;

wait;

end process;

-- Stimulus process

process

begin

RESET <= '1'; -- Assert reset initially

wait for 20 ns; -- Wait for a few clock cycles

RESET <= '0'; -- Deassert reset

-- Test Case 1: Multiply A = 0010, B = 0011

A <= "0010";

B <= "0011";

wait for CLK\_PERIOD; -- Wait for one clock cycle

-- Test Case 2: Multiply A = 1100, B = 0101

A <= "1100";

B <= "0101";

wait for CLK\_PERIOD; -- Wait for one clock cycle

-- Add more test cases as needed...

report "Simulation completed" severity note;

wait;

end process;


-- Instantiate the 4-Bit Multiplier component


Multiplier\_inst : FourBitMultiplier

port map (

CLK => CLK,

RESET

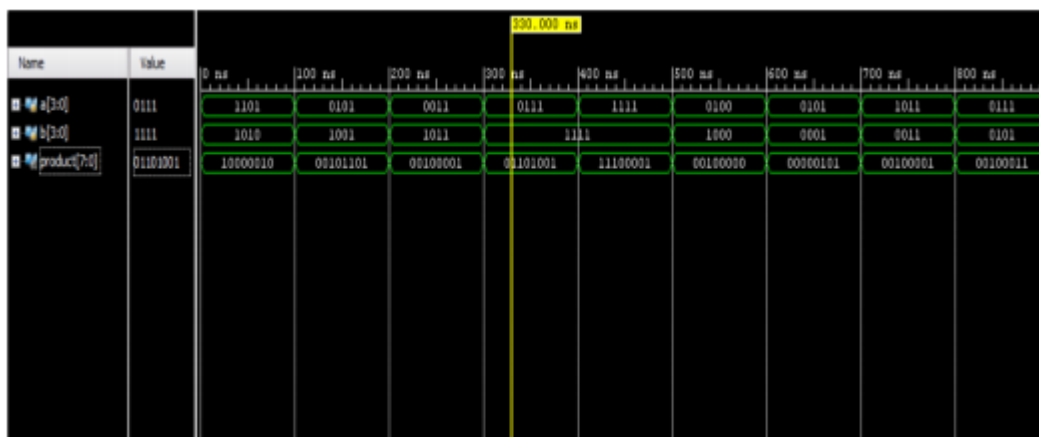

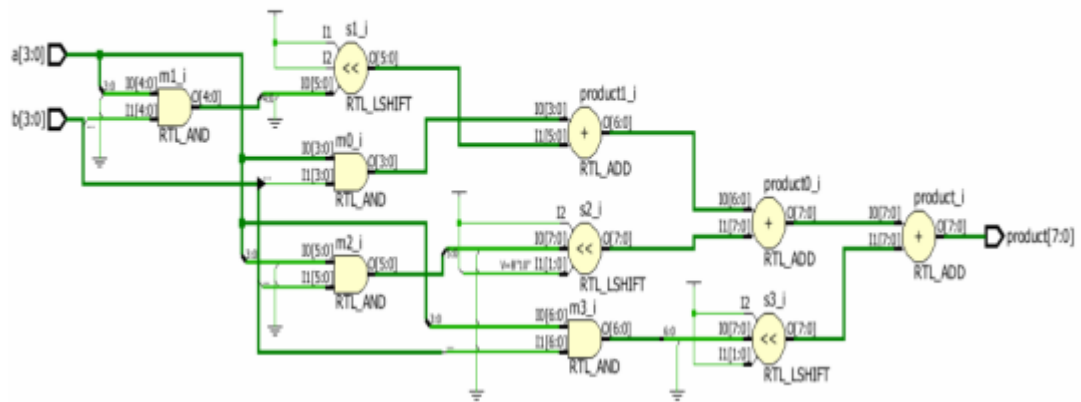

## DAY 19: FIXED POINT DIVISION

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;

entity FixedPointDivider is
    Port (
        Dividend : in STD_LOGIC_VECTOR(31 downto 0); -- 32-bit input
        Divisor   : in STD_LOGIC_VECTOR(31 downto 0); -- 32-bit input
        Quotient  : out STD_LOGIC_VECTOR(31 downto 0) -- 32-bit output
    );
end FixedPointDivider;

architecture Behavioral of FixedPointDivider is
    constant FRACTIONAL_BITS : integer := 24; -- Number of fractional bits
    constant SHIFT_AMOUNT    : integer := 24; -- Shift amount for
division

    signal dividend_reg : STD_LOGIC_VECTOR(55 downto 0); -- Register for
dividend
    signal quotient_reg : STD_LOGIC_VECTOR(31 downto 0); -- Register for
quotient

    signal counter      : integer := 0; -- Counter for division loop
begin
    process(Dividend, Divisor)
    begin
        if Divisor = "00000000000000000000000000000000" then
            Quotient <= (others => 'X'); -- Handle division by zero
        else
            dividend_reg <= Dividend & (others => '0'); -- Shift dividend left by
FRACTIONAL_BITS
            quotient_reg <= (others => '0'); -- Initialize quotient

            for counter in 0 to 31 loop
                dividend_reg <= '0' & dividend_reg(55 downto 1); -- Shift dividend
left
                quotient_reg <= quotient_reg(30 downto 0) & '0'; -- Shift quotient
left

                if dividend_reg(55 downto 32) >= Divisor then
                    quotient_reg(31) <= '1'; -- Set quotient bit
```

```

        dividend_reg(55 downto 32) <= dividend_reg(55 downto 32) -
        Divisor; -- Subtract divisor
        end if;
    end loop;

    Quotient <= quotient_reg; -- Output quotient
    end if;
end process;
end Behavioral;

```

Test bench

```

-- Test bench for FIXED POINT DIVISION
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity test_FixedPoint_Division is
end test_FixedPoint_Division;

architecture testbench of test_FixedPoint_Division is
    -- Constants
    constant CLK_PERIOD: time := 10 ns; -- Clock period (adjust as needed)

    -- Signals
    signal CLK: std_logic := '0';          -- Clock input
    signal RESET: std_logic := '0';        -- Reset input
    signal NUMERATOR, DENOMINATOR: std_logic_vector(7 downto 0); -- 8-bit
    inputs
    signal DIV_RESULT: std_logic_vector(15 downto 0); -- Result output

    -- Instantiate the Fixed Point Division component
    component FixedPointDivision
        Port (
            CLK : in  STD_LOGIC;
            RESET : in  STD_LOGIC;
            NUMERATOR, DENOMINATOR : in  STD_LOGIC_VECTOR(7 downto 0);
            DIV_RESULT : out STD_LOGIC_VECTOR(15 downto 0)
        );
    end component;

    -- Clock generation process
    process

```



```

begin
    while now < 1000 ns loop -- Simulate for 1000 ns (adjust as needed)
        CLK <= '0';
        wait for CLK_PERIOD / 2;
        CLK <= '1';
        wait for CLK_PERIOD / 2;
    end loop;
    wait;
end process;

-- Stimulus process
process
begin
    RESET <= '1'; -- Assert reset initially

    wait for 20 ns; -- Wait for a few clock cycles

    RESET <= '0'; -- Deassert reset

    -- Test Case 1: Divide NUMERATOR = 10010010, DENOMINATOR =
00101101
    NUMERATOR <= "10010010";
    DENOMINATOR <= "00101101";
    wait for CLK_PERIOD; -- Wait for one clock cycle

    -- Test Case 2: Divide NUMERATOR = 11001100, DENOMINATOR =
00110011
    NUMERATOR <= "11001100";
    DENOMINATOR <= "00110011";
    wait for CLK_PERIOD; -- Wait for one clock cycle

    -- Add more test cases as needed...

    report "Simulation completed" severity note;
    wait;
end process;

-- Instantiate the Fixed Point Division component
Division_inst : FixedPointDivision
    port map (
        CLK => CLK,
        RESET => RESET,
        NUMERATOR => NUMERATOR,
        DENOMINATOR => DENOMINATOR,

```

```



DIV_RESULT => DIV_RESULT
);

```

```

end testbench;

```

 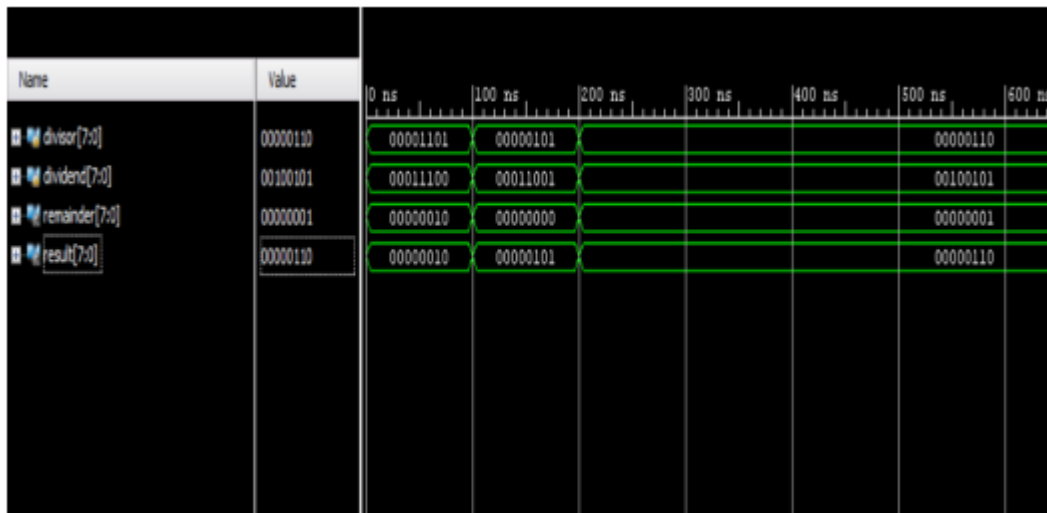

## DAY 20: MASTER SLAVE JK FLIP FLOP

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity JK_FlipFlop is
    Port (
        J, K, CLK, RESET : in STD_LOGIC;
        Q, Qn : out STD_LOGIC
    );
end JK_FlipFlop;

architecture Behavioral of JK_FlipFlop is
    signal state : STD_LOGIC := '0';
begin
    process(CLK, RESET)
    begin
        if RESET = '1' then
            state <= '0';
        elsif rising_edge(CLK) then
            if J = '0' and K = '0' then
                state <= state; -- No change
            elsif J = '0' and K = '1' then
                state <= '0'; -- Reset (Q = 0)
            elsif J = '1' and K = '0' then
                state <= '1'; -- Set (Q = 1)
            else
                state <= not state; -- Toggle
            end if;
        end if;
    end process;

    Q <= state;
    Qn <= not state;
end Behavioral;
```

## Test bench

-- Test bench for MASTER-SLAVE JK FLIP-FLOP

library IEEE;

use IEEE.STD\_LOGIC\_1164.ALL;

entity test\_MasterSlave\_JK\_FlipFlop is

end test\_MasterSlave\_JK\_FlipFlop;

architecture testbench of test\_MasterSlave\_JK\_FlipFlop is

-- Constants

constant CLK\_PERIOD: time := 10 ns; -- Clock period (adjust as needed)

-- Signals

signal CLK: std\_logic := '0'; -- Clock input

signal RESET: std\_logic := '0'; -- Reset input

signal J, K: std\_logic := '0'; -- J and K inputs

signal Q, Qn: std\_logic; -- Outputs

-- Instantiate the Master-Slave JK Flip-Flop component  
component MasterSlaveJKFlipFlop

Port (

CLK : in STD\_LOGIC;

RESET : in STD\_LOGIC;

J, K : in STD\_LOGIC;

Q, Qn : out STD\_LOGIC

);

end component;

-- Clock generation process

process

begin

while now < 1000 ns loop -- Simulate for 1000 ns (adjust as needed)

CLK <= '0';

wait for CLK\_PERIOD / 2;

CLK <= '1';

wait for CLK\_PERIOD / 2;

end loop;

wait;

end process;

```

-- Stimulus process
process
begin
    RESET <= '1'; -- Assert reset initially

    wait for 20 ns; -- Wait for a few clock cycles

    RESET <= '0'; -- Deassert reset

    -- Test Case 1: Set J and K to toggle Q
    J <= '1';
    K <= '1';
    wait for 2 * CLK_PERIOD; -- Wait for two clock cycles

    -- Test Case 2: Set J to '1' and K to '0' to set Q
    J <= '1';
    K <= '0';
    wait for 2 * CLK_PERIOD; -- Wait for two clock cycles


    -- Add more test cases as needed...

    report "Simulation completed" severity note;
    wait;
end process;

-- Instantiate the Master-Slave JK Flip-Flop component
FlipFlop_inst : MasterSlaveJKFlipFlop
    port map (
        CLK => CLK,
        RESET => RESET,
        J => J,
        K => K,
        Q => Q,
        Qn => Qn
    );

end testbench;

```

 

## DAY 21: POSITIVE EDGE DETECTOR

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity PositiveEdgeDetector is
    Port (
        CLK : in STD_LOGIC;
        RISING_EDGE : out STD_LOGIC
    );
end PositiveEdgeDetector;

architecture Behavioral of PositiveEdgeDetector is
    signal prev_clk : STD_LOGIC := '0';
begin
    process(CLK)
    begin
        if rising_edge(CLK) then
            RISING_EDGE <= (CLK and (not prev_clk));
            prev_clk <= CLK;
        else
            RISING_EDGE <= '0';
        end if;
    end process;
end Behavioral;
```

Test bench

```
-- Test bench for POSITIVE EDGE DETECTOR
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity test_PositiveEdge_Detector is
end test_PositiveEdge_Detector;

architecture testbench of test_PositiveEdge_Detector is
    -- Constants
    constant CLK_PERIOD: time := 10 ns; -- Clock period (adjust as needed)

    -- Signals
```

```

signal CLK: std_logic := '0';           -- Clock input
signal RESET: std_logic := '0';        -- Reset input
signal D: std_logic;                   -- Input signal
signal POS_EDGE_DETECT: std_logic;     -- Output signal

```

```

-- Instantiate the Positive Edge Detector component
component PositiveEdgeDetector

```

```

    Port (
        CLK : in  STD_LOGIC;
        RESET : in  STD_LOGIC;
        D : in  STD_LOGIC;
        POS_EDGE_DETECT : out STD_LOGIC
    );

```

```

end component;

```

```

-- Clock generation process

```

```

process

```

```

begin

```

```

    while now < 1000 ns loop -- Simulate for 1000 ns (adjust as needed)

```

```

        CLK <= '0';

```

```

        wait for CLK_PERIOD / 2;

```

```

        CLK <= '1';

```

```

        wait for CLK_PERIOD / 2;

```

```

    end loop;

```

```

    wait;

```

```

end process;

```

```

-- Stimulus process

```

```

process

```





## DAY 22: BCD ADDER

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;

entity BCD_Adder is
    Port (
        A, B : in STD_LOGIC_VECTOR(3 downto 0);
        SUM : out STD_LOGIC_VECTOR(3 downto 0);
        COUT : out STD_LOGIC
    );
end BCD_Adder;

architecture Behavioral of BCD_Adder is
begin
    process(A, B)
    begin
        SUM <= A + B;
        if SUM > "1001" then
            SUM <= SUM + "0110";
        end if;
        COUT <= '1' when SUM > "1001" else '0';
    end process;
end Behavioral;
```

### Test bench

```
-- Test bench for BCD ADDER
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity test_BCD_Adder is
end test_BCD_Adder;

architecture testbench of test_BCD_Adder is
    -- Constants
    constant CLK_PERIOD: time := 10 ns; -- Clock period (adjust as needed)

    -- Signals
    signal CLK: std_logic := '0';          -- Clock input
    signal RESET: std_logic := '0';        -- Reset input
```

```
signal A, B: std_logic_vector(3 downto 0); -- 4-bit BCD inputs
signal SUM: std_logic_vector(3 downto 0);      -- Sum output
signal CARRY_OUT: std_logic;                  -- Carry out
```

```
-- Instantiate the BCD Adder component
```

```
component BCDAdder
```

```
    Port (
        CLK : in  STD_LOGIC;
        RESET : in  STD_LOGIC;
        A, B : in  STD_LOGIC_VECTOR(3 downto 0);
        SUM : out STD_LOGIC_VECTOR(3 downto 0);
        CARRY_OUT : out STD_LOGIC
    );
```

```
end component;
```

```
-- Clock generation process
```

```
process
```

```
begin
```

```
    while now < 1000 ns loop -- Simulate for 1000 ns (adjust as needed)
```

```
        CLK <= '0';
```

```
        wait for CLK_PERIOD / 2;
```

```
        CLK <= '1';
```

```
        wait for CLK_PERIOD / 2;
```

```
    end loop;
```

```
    wait;
```

```
end process;
```

```
-- Stimulus process
```

```
process
```

```
begin
```

```
    RESET <= '1'; -- Assert reset initially
```

```
    wait for 20 ns; -- Wait for a few clock cycles
```

```
    RESET <= '0'; -- Deassert reset
```

```
    -- Test Case 1: A = 0010, B = 0011
```

```
    A <= "0010";
```

```
    B <= "0011";
```

```
    wait for CLK_PERIOD; -- Wait for one clock cycle
```

```
    -- Test Case 2: A = 1100, B = 0101
```

```
    A <= "1100";
```

```
    B <= "0101";
```

```
wait for CLK_PERIOD; -- Wait for one clock cycle
```

```
-- Add more test cases as needed...
```

```
report "Simulation completed" severity note;
```

```
wait;
```

```
end process;
```

```
-- Instantiate the BCD Adder component
```

```
BCD_Adder_inst : BCDAdder
```

```
port map (
```

```
CLK => CLK,
```

```
RESET => RESET,
```

```
A => A,
```

```
B => B,
```


```
SUM => SUM,
```

```
CARRY_OUT => CARRY_OUT
```

```
);
```

```
end testbench;
```



 

## DAY 23: 4-BIT CARRY SELECT ADDER

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;

entity CarrySelectAdder is
    Port (
        A, B : in STD_LOGIC_VECTOR(3 downto 0);
        Cin : in STD_LOGIC;
        Sum : out STD_LOGIC_VECTOR(3 downto 0);
        Cout : out STD_LOGIC
    );
end CarrySelectAdder;

architecture Behavioral of CarrySelectAdder is
    signal G, P, G1, P1, G2, P2, C1, C2 : STD_LOGIC_VECTOR(3 downto 0);
begin
    G <= (others => '0');
    P <= (others => '0');
    G1 <= A and B;
    P1 <= A xor B;
    G2 <= G1 and Cin;
    P2 <= P1 or G2;
    C1 <= G1 or (P1 and Cin);
    C2 <= G2 or (P2 and G);
    Sum <= P2 xor G;
    Cout <= C2;
end Behavioral;
```

### Test bench

-- Test bench for 4-BIT CARRY SELECT ADDER

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity test_4Bit_CarrySelect_Adder is
end test_4Bit_CarrySelect_Adder;

architecture testbench of test_4Bit_CarrySelect_Adder is
```

```

-- Constants
constant CLK_PERIOD: time := 10 ns; -- Clock period (adjust as needed)

-- Signals
signal CLK: std_logic := '0';          -- Clock input
signal RESET: std_logic := '0';        -- Reset input
signal A, B: std_logic_vector(3 downto 0); -- 4-bit inputs A and B
signal SUM: std_logic_vector(3 downto 0); -- Sum output
signal CARRY_OUT: std_logic;           -- Carry out

-- Instantiate the 4-Bit Carry Select Adder component
component FourBitCarrySelectAdder
  Port (
    CLK : in  STD_LOGIC;
    RESET : in  STD_LOGIC;
    A, B : in  STD_LOGIC_VECTOR(3 downto 0);
    SUM : out STD_LOGIC_VECTOR(3 downto 0);
    CARRY_OUT : out STD_LOGIC
  );
end component;

-- Clock generation process
process
begin
  while now < 1000 ns loop -- Simulate for 1000 ns (adjust as needed)
    CLK <= '0';
    wait for CLK_PERIOD / 2;
    CLK <= '1';
    wait for CLK_PERIOD / 2;
  end loop;
  wait;
end process;

-- Stimulus process
process
begin
  RESET <= '1'; -- Assert reset initially

  wait for 20 ns; -- Wait for a few clock cycles

  RESET <= '0'; -- Deassert reset

  -- Test Case 1: A = 0010, B = 0011
  A <= "0010";

```

```
B <= "0011";
wait for CLK_PERIOD; -- Wait for one clock cycle
```

```
-- Test Case 2: A = 1100, B = 0101
A <= "1100";
B <= "0101";
wait for CLK_PERIOD; -- Wait for one clock cycle
```


**-- Add more test cases as needed...**


```

report "Simulation completed" severity note;
wait;
end process;
```

```
-- Instantiate the 4-Bit Carry Select Adder component
Carry_Select_Adder_inst : FourBitCarrySelectAdder
    port map (
        CLK => CLK,
        RESET => RESET,
        A => A,
        B => B,
        SUM => SUM,
        CARRY_OUT => CARRY_OUT
    );
```

```
end testbench;
```

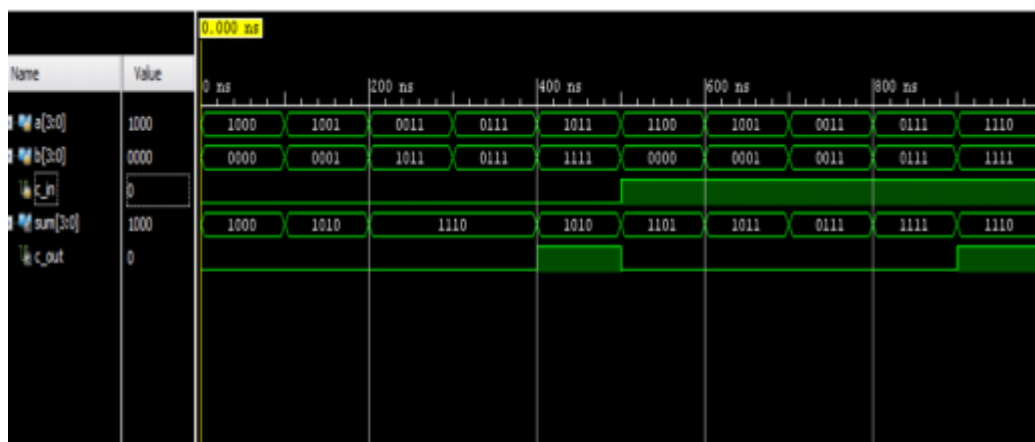

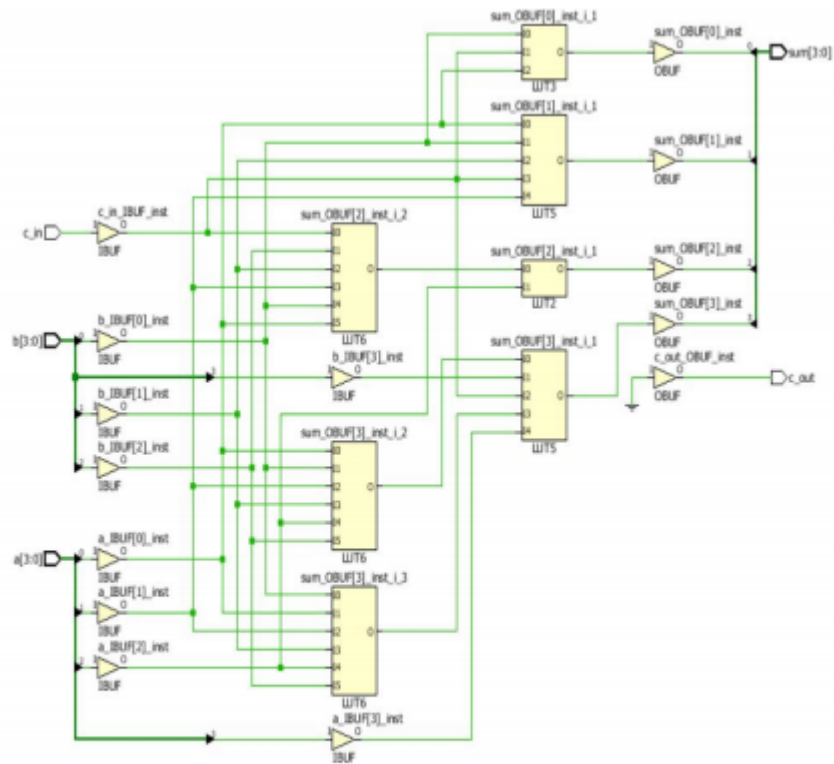



## DAY 24: MOORE FSM 1010 SEQUENCE DETECTOR

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity MooreSequenceDetector is
    Port (
        CLK, RESET : in STD_LOGIC;
        SEQ_OUT  : out STD_LOGIC
    );
end MooreSequenceDetector;

architecture Behavioral of MooreSequenceDetector is
    type State_Type is (S0, S1, S2, S3, S4);
    signal Current_State, Next_State : State_Type := S0;
begin
    process(CLK, RESET)
    begin
        if RESET = '1' then
            Current_State <= S0;
        elsif rising_edge(CLK) then
            Current_State <= Next_State;
        end if;
    end process;

    process(Current_State)
    begin
        case Current_State is
            when S0 =>
                if RESET = '1' then
                    SEQ_OUT <= '0';
                else
                    SEQ_OUT <= '0';
                end if;
                Next_State <= S1;
            when S1 =>
                SEQ_OUT <= '0';
                if RESET = '1' then
                    Next_State <= S0;
                elsif SEQ_OUT = '1' then
                    Next_State <= S2;
                else
```

```

        Next_State <= S1;
    end if;
when S2 =>
    SEQ_OUT <= '0';
    if SEQ_OUT = '0' then
        Next_State <= S1;
    else
        Next_State <= S3;
    end if;
when S3 =>
    SEQ_OUT <= '0';
    if SEQ_OUT = '1' then
        Next_State <= S4;
    else
        Next_State <= S1;
    end if;
when S4 =>
    SEQ_OUT <= '1';
    if SEQ_OUT = '0' then
        Next_State <= S1;
    else
        Next_State <= S4;
    end if;
when others =>
    Next_State <= S0;
end case;
end process;
end Behavioral;

```

## Test bench

-- Test bench for MOORE FSM 1010 SEQUENCE DETECTOR

library IEEE;

use IEEE.STD\_LOGIC\_1164.ALL;

entity test\_Moore\_SequenceDetector is

end test\_Moore\_SequenceDetector;

architecture testbench of test\_Moore\_SequenceDetector is

-- Constants

constant CLK\_PERIOD: time := 10 ns; -- Clock period (adjust as needed)

```

-- Signals
signal CLK: std_logic := '0';           -- Clock input
signal RESET: std_logic := '0';         -- Reset input
signal INPUT: std_logic := '0';         -- Input signal
signal OUTPUT: std_logic;               -- Output signal

-- Instantiate the Moore Sequence Detector component
component MooreSequenceDetector
    Port (
        CLK : in  STD_LOGIC;
        RESET : in  STD_LOGIC;
        INPUT : in  STD_LOGIC;
        OUTPUT : out STD_LOGIC
    );
end component;

-- Clock generation process
process
begin
    while now < 1000 ns loop -- Simulate for 1000 ns (adjust as needed)
        CLK <= '0';
        wait for CLK_PERIOD / 2;
        CLK <= '1';
        wait for CLK_PERIOD / 2;
    end loop;
    wait;
end process;

-- Stimulus process
process
begin
    RESET <= '1'; -- Assert reset initially

    wait for 20 ns; -- Wait for a few clock cycles

    RESET <= '0'; -- Deassert reset

    -- Test Case 1: Input sequence 1010
    INPUT <= '1';
    wait for CLK_PERIOD; -- Wait for one clock cycle
    INPUT <= '0';
    wait for CLK_PERIOD; -- Wait for one clock cycle
    INPUT <= '1';
    wait for CLK_PERIOD; -- Wait for one clock cycle

```

```
INPUT <= '0';
wait for CLK_PERIOD; -- Wait for one clock cycle
```

### -- Test Case 2: Input sequence 1101

```

INPUT <= '1';
wait for CLK_PERIOD; -- Wait for one clock cycle
INPUT <= '1';
wait for CLK_PERIOD; -- Wait for one clock cycle
INPUT <= '0';
wait for CLK_PERIOD; -- Wait for one clock cycle
INPUT <= '1';
wait for CLK_PERIOD; -- Wait for one clock cycle

```

**-- Add more test cases as needed...**

```

report "Simulation completed" severity note;
wait;
end process;


```

### -- Instantiate the Moore Sequence Detector component

**Sequence\_Detector\_inst : MooreSequenceDetector**

```
port map (
  CLK => CLK,
  RESET => RESET,
  INPUT => INPUT,
  OUTPUT => OUTPUT
);
```

```
end testbench;
```

 

## DAY 25: N:1 MUX

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity MUX_Nto1 is
    Port (
        A, B, C, D : in STD_LOGIC;
        SEL : in STD_LOGIC_VECTOR(1 downto 0);
        Y : out STD_LOGIC
    );
end MUX_Nto1;
```

architecture Behavioral of MUX\_Nto1 is

### Test bench

```
-- Test bench for N:1 MUX
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity test_Nto1_MUX is
end test_Nto1_MUX;

architecture testbench of test_Nto1_MUX is
    -- Constants
    constant CLK_PERIOD: time := 10 ns; -- Clock period (adjust as needed)

    -- Signals
    signal CLK: std_logic := '0';          -- Clock input
    signal RESET: std_logic := '0';        -- Reset input
    signal SELECT: std_logic_vector(1 downto 0); -- Select inputs
    signal DATA_IN: std_logic_vector(3 downto 0); -- Data inputs
    signal DATA_OUT: std_logic;           -- Data output

    -- Instantiate the N:1 MUX component
    component Nto1MUX
```

```

Port (
  CLK : in  STD_LOGIC;
  RESET : in  STD_LOGIC;
  SELECT : in  STD_LOGIC_VECTOR(1 downto 0);
  DATA_IN : in  STD_LOGIC_VECTOR(3 downto 0);
  DATA_OUT : out STD_LOGIC
);
end component;

-- Clock generation process
process
begin
  while now < 1000 ns loop -- Simulate for 1000 ns (adjust as needed)
    CLK <= '0';
    wait for CLK_PERIOD / 2;
    CLK <= '1';
    wait for CLK_PERIOD / 2;
  end loop;
  wait;
end process;

-- Stimulus process
process
begin
  RESET <= '1'; -- Assert reset initially

  wait for 20 ns; -- Wait for a few clock cycles

  RESET <= '0'; -- Deassert reset

  -- Test Case 1: SELECT = "00", DATA_IN = "1010"
  SELECT <= "00";
  DATA_IN <= "1010";
  wait for CLK_PERIOD; -- Wait for one clock cycle

  -- Test Case 2: SELECT = "01", DATA_IN = "0011"
  SELECT <= "01";
  DATA_IN <= "0011";
  wait for CLK_PERIOD; -- Wait for one clock cycle

  -- Add more test cases as needed...

  report "Simulation completed" severity note;
  wait;

```

```
end process;
```

```
-- Instantiate the N:1 MUX component
```

```
MUX_inst : Nto1MUX
```

```
port map (
```

```
CLK => CLK,
```

```
RESET => RESET,
```

```
SELECT => SELECT,
```

```
DATA_IN => DATA_IN,
```

```
DATA_OUT => DATA_OUT
```

```
);
```

```
end testbench;
```



